

CONVEYOR BELT WITH COUNTER

يوسف إبراهيم عبد العزيز السيد ندا

احمد جمال السيد أبو الخير

محمود مصطفى عطية مصطفى

هشام محمد بدير المرسي

محمد عمرو احمد فوزي

احمد إبراهيم عبد الحميد

تحت اشراف:

د/ عماد بدري

• Introduction

This system is designed to demonstrate the operation of a conveyor belt associated with a counting circuit where upon the passing of each box (or any object on the belt) a signal is transmitted and decoded to a circuit. The count will be displayed by a 7-segment display.


• Operation

1. The conveyor belt is operated by a **5-volt dc motor** at the beginning of operation.
2. An **IR sensor** is set up to detect any passing object (box, ball ,...etc.).
3. As long as no objects have passed, the display shows 0 until the detection of an object by the IR sensor.
4. When this detection occurs an **NE555 timer** circuit starts counting and sends clocks to the counter.
5. Upon reaching the count of 5 this means that the operation needs to halt, and this happens simultaneously.
6. The **Nand gate** sends a signal to stop the motor and the buzzer alerts us to this.
7. To start over the operation we have a **button**, upon pressing the button a signal is sent to a S-R latch that drives the motor and the operation is repeated.

- **Components**

- 7 segment BCD
- 74HC160 Decade counter
- 74HC47
- Push button and Selector button
- cap 10 uF
- cap10 nF
- IR sensor
- LED
- 10 k Resistor
- 100 Kilo-ohm potentiometer
- 220 ohm
- Nand gate
- Nor gate
- Relay
- DC motor
- NE555

• Schematics

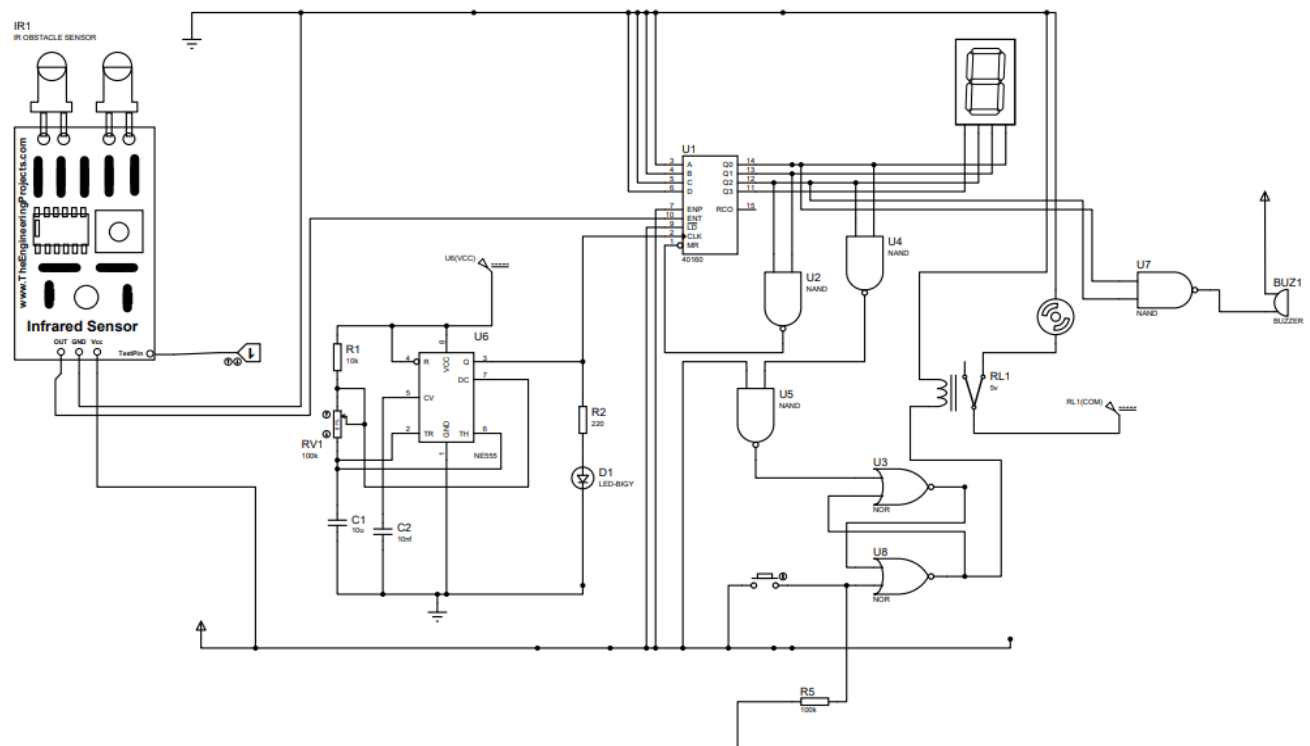

• Proteus Simulation

