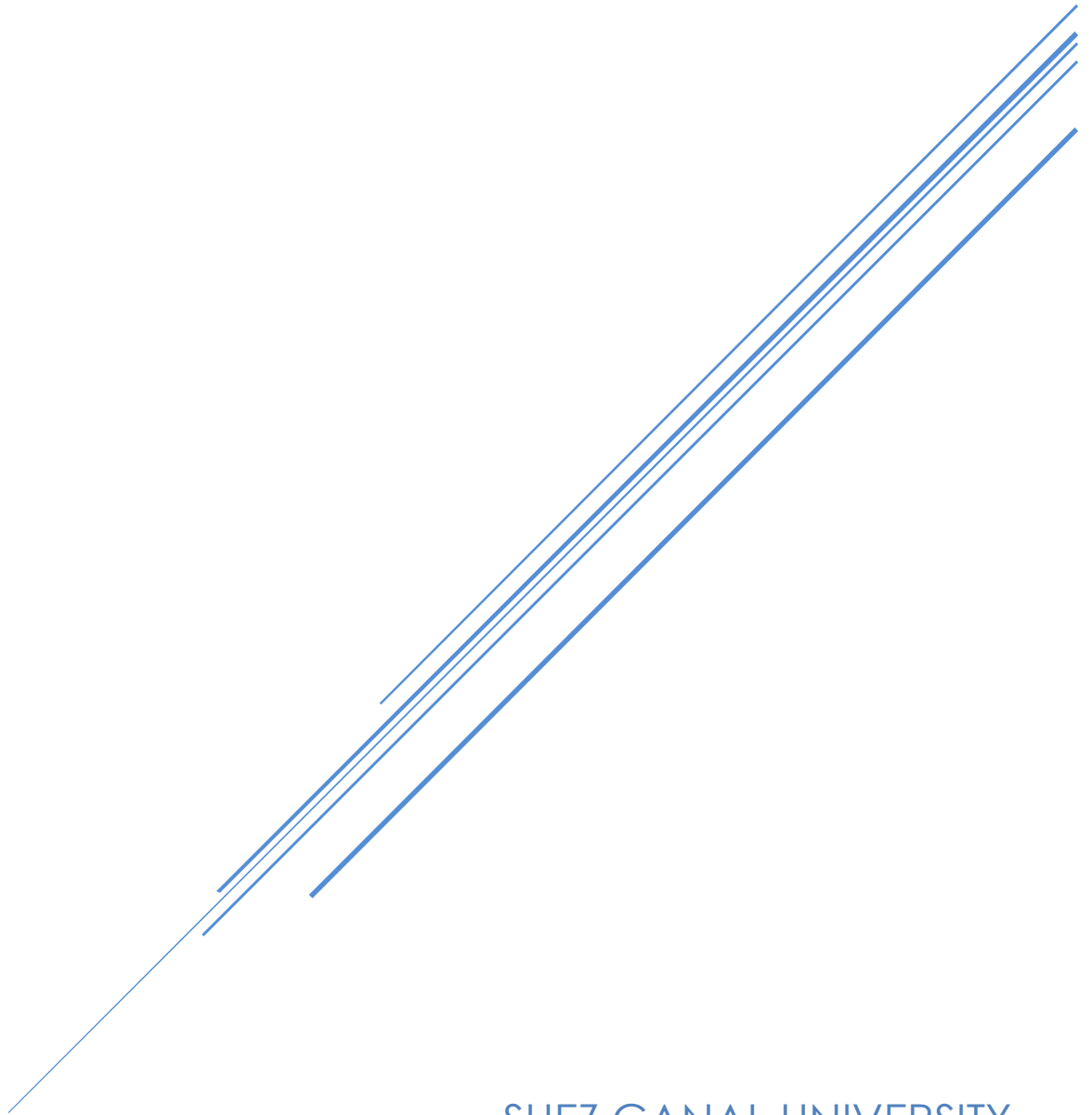




# POWER ELECTRONICS MATLAB





SUEZ CANAL UNIVERSITY

Yossef ibrahim Abd El Aziz EL Sayed Nada

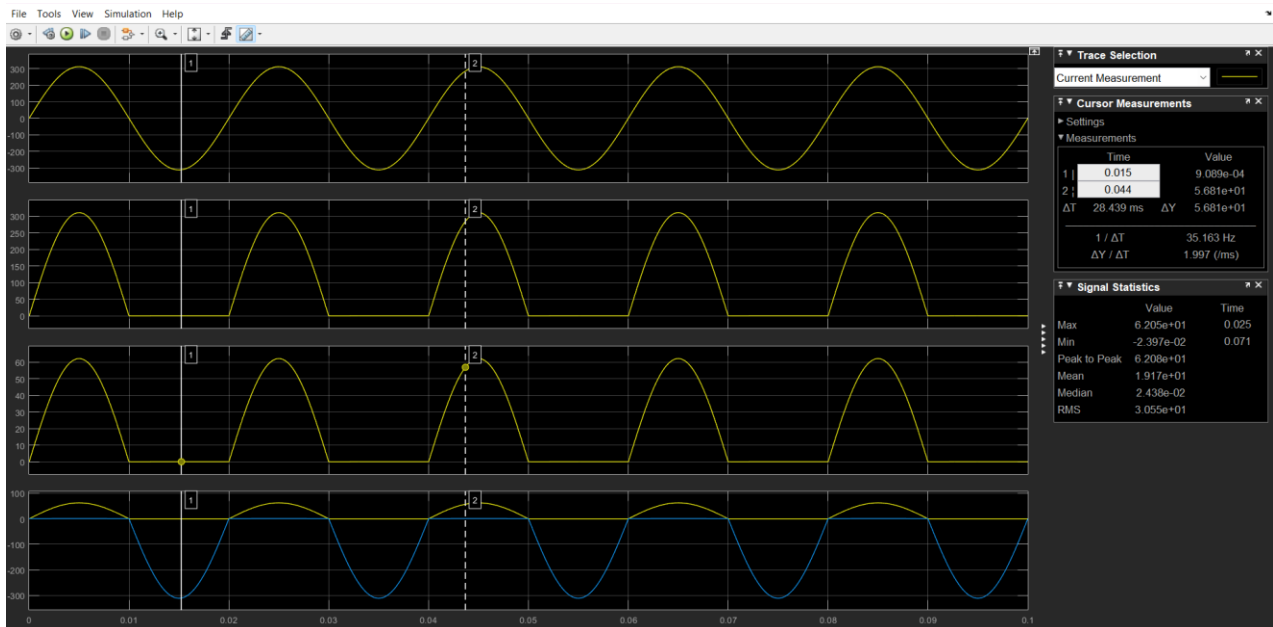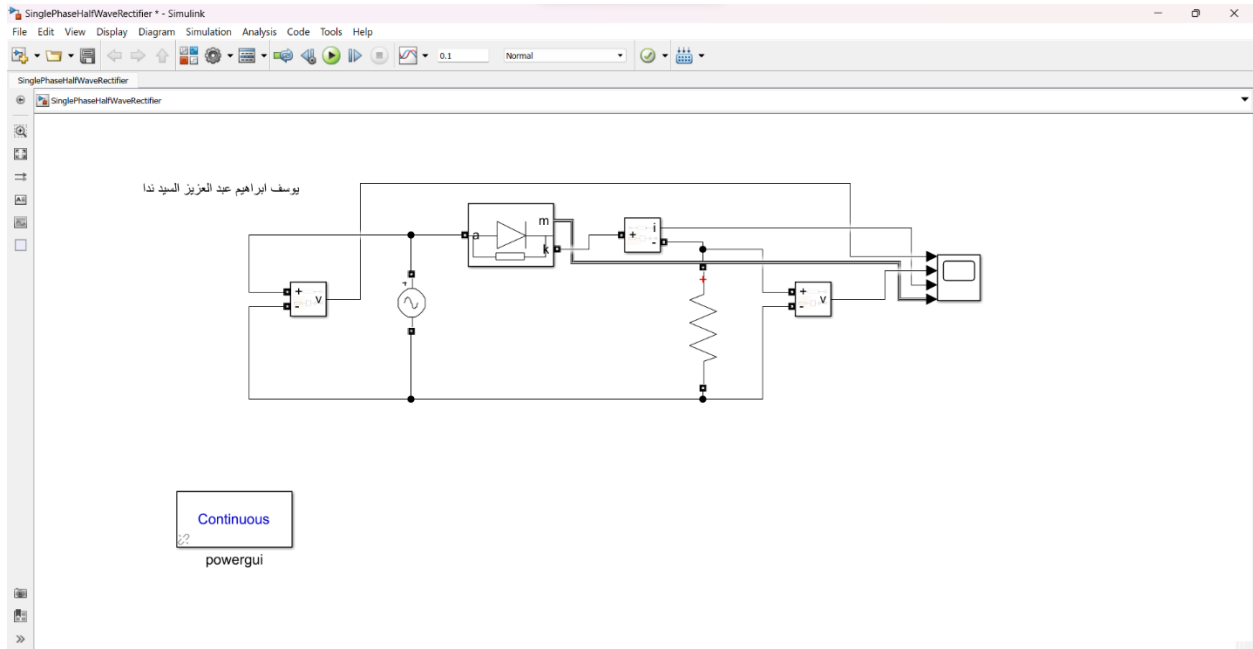
## Single phase Half wave rectifier R\_load:



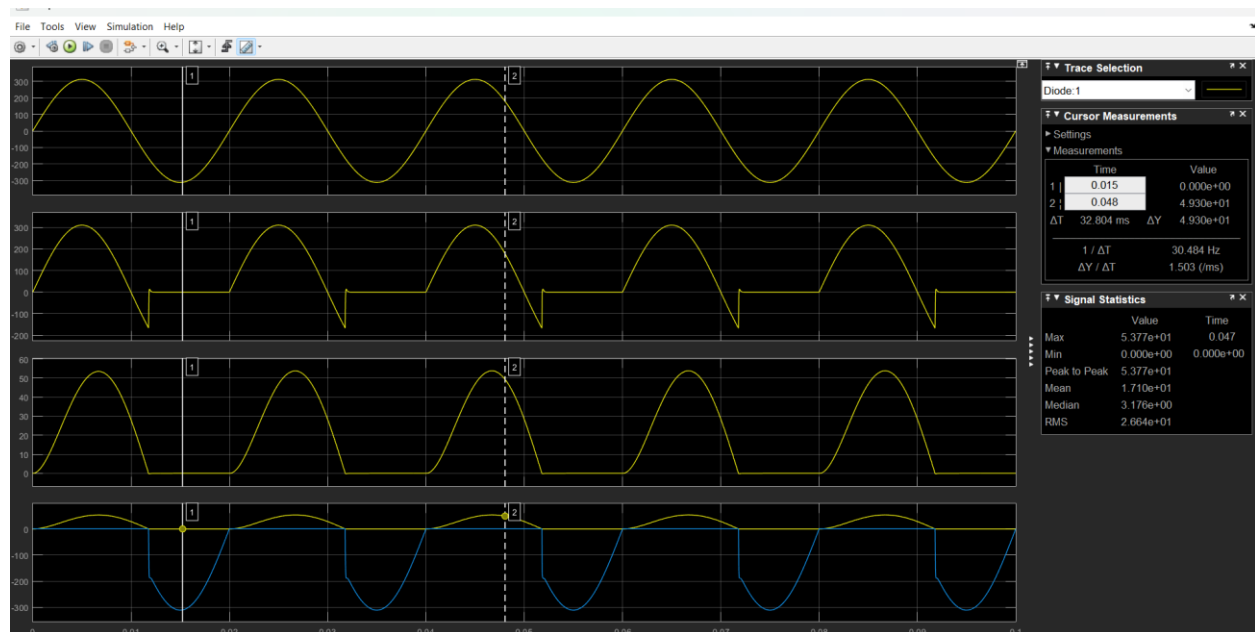
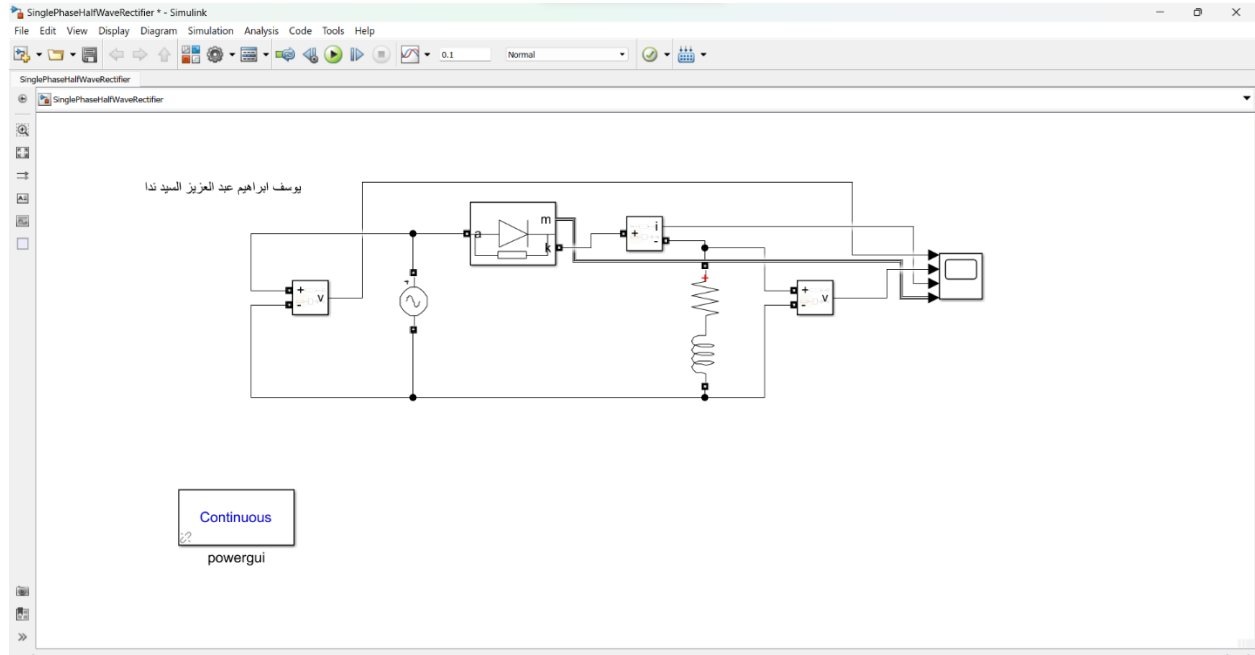
## Single phase Half wave rectifier R&L\_load:




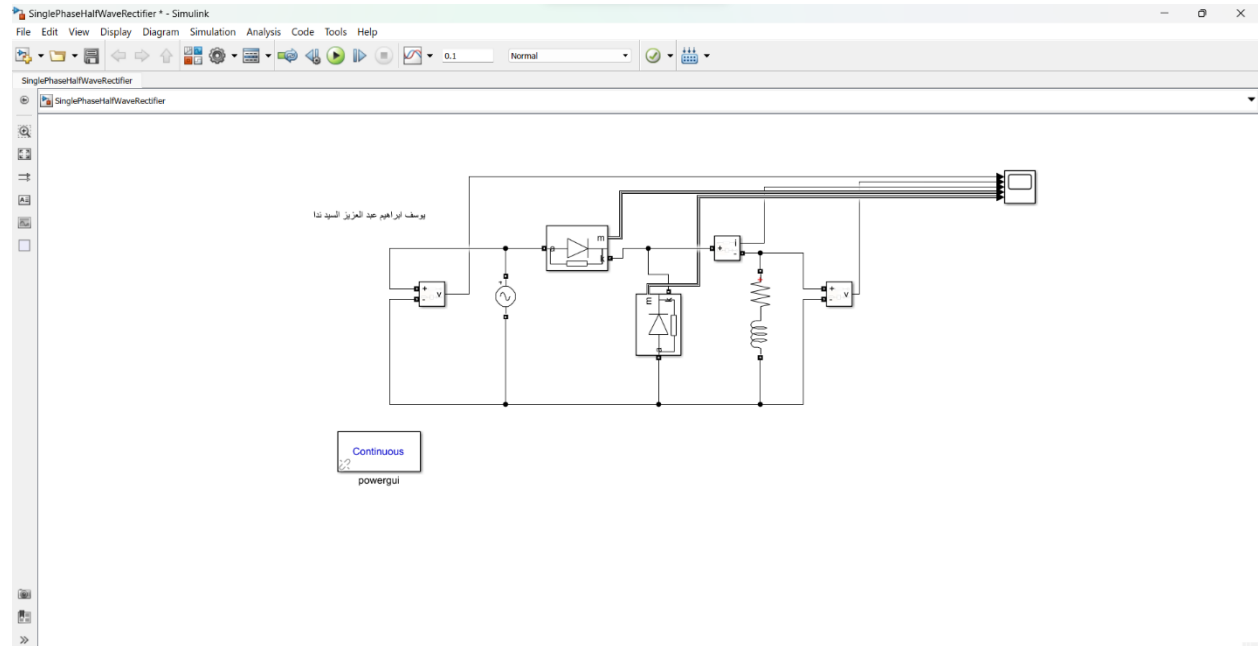
# Single phase Half wave rectifier R&L\_load + Free wheeling diode :



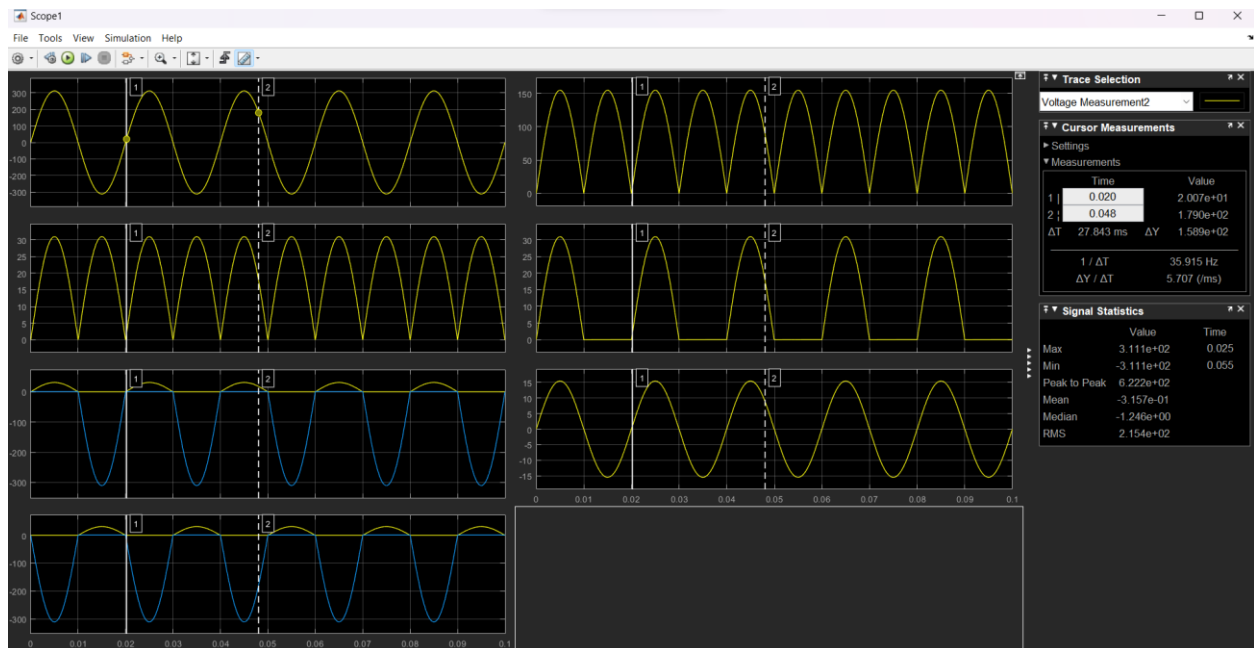
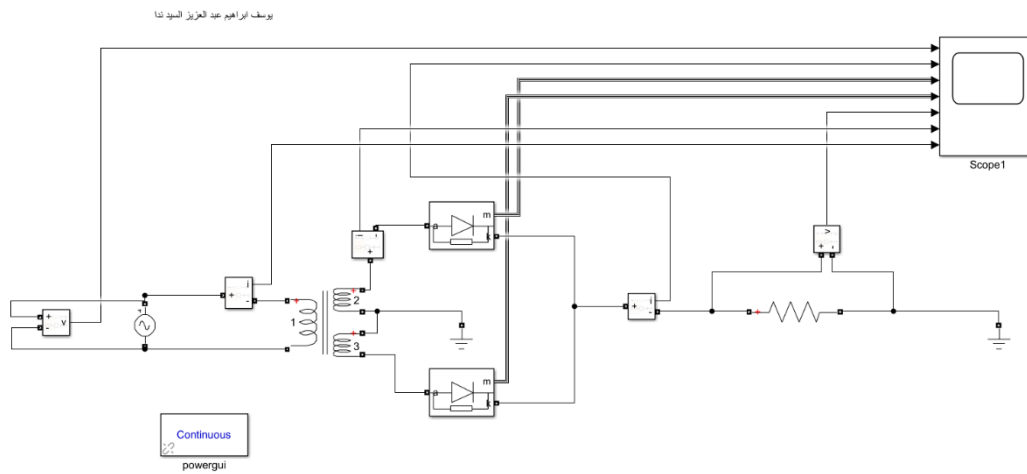
# Single phase Full wave rectifier: Center tapped $\rightarrow R_{load}$ :



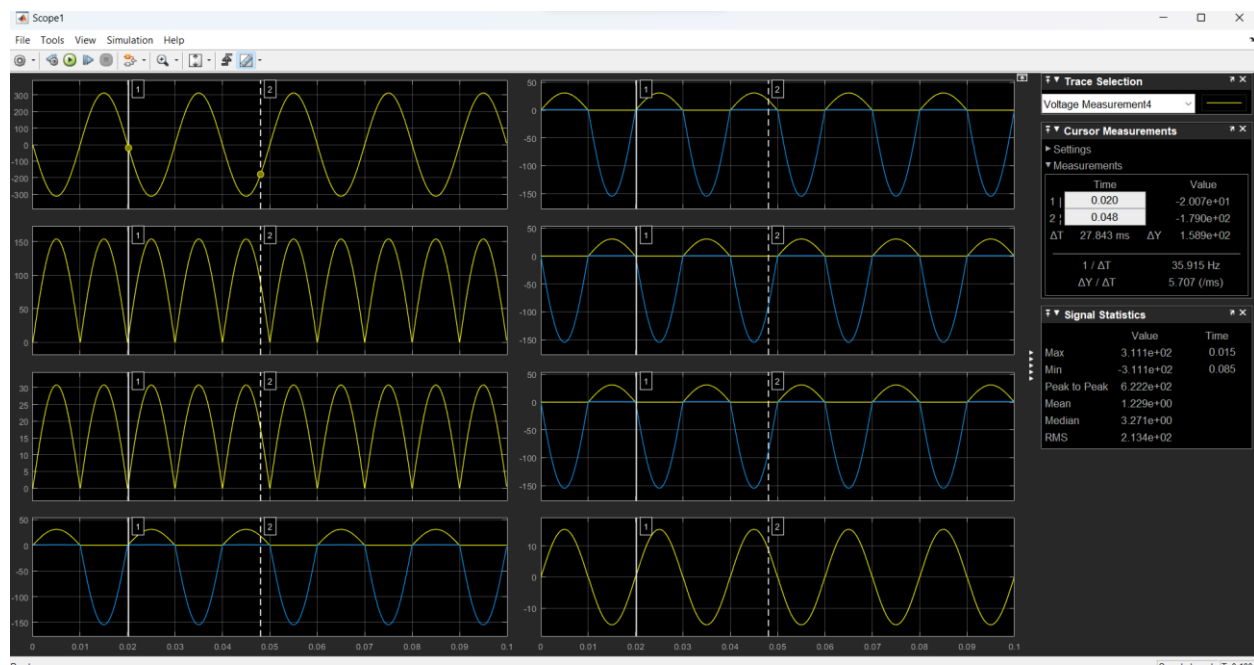
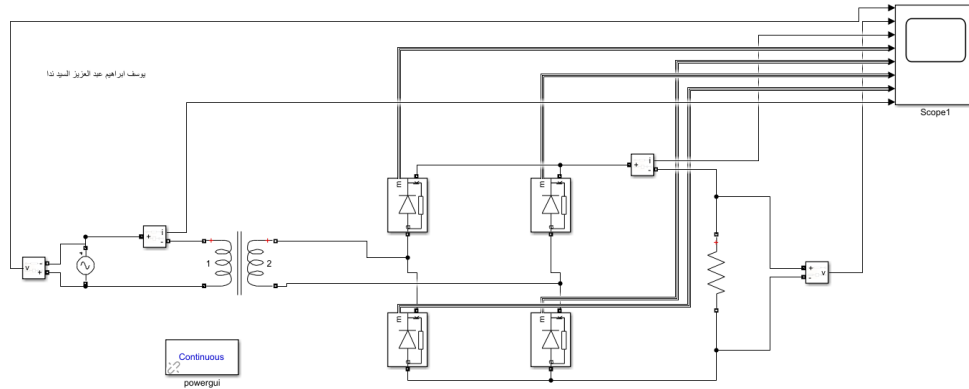
Single phase Full wave rectifier: Bridge  $\rightarrow$  R<sub>load</sub>:


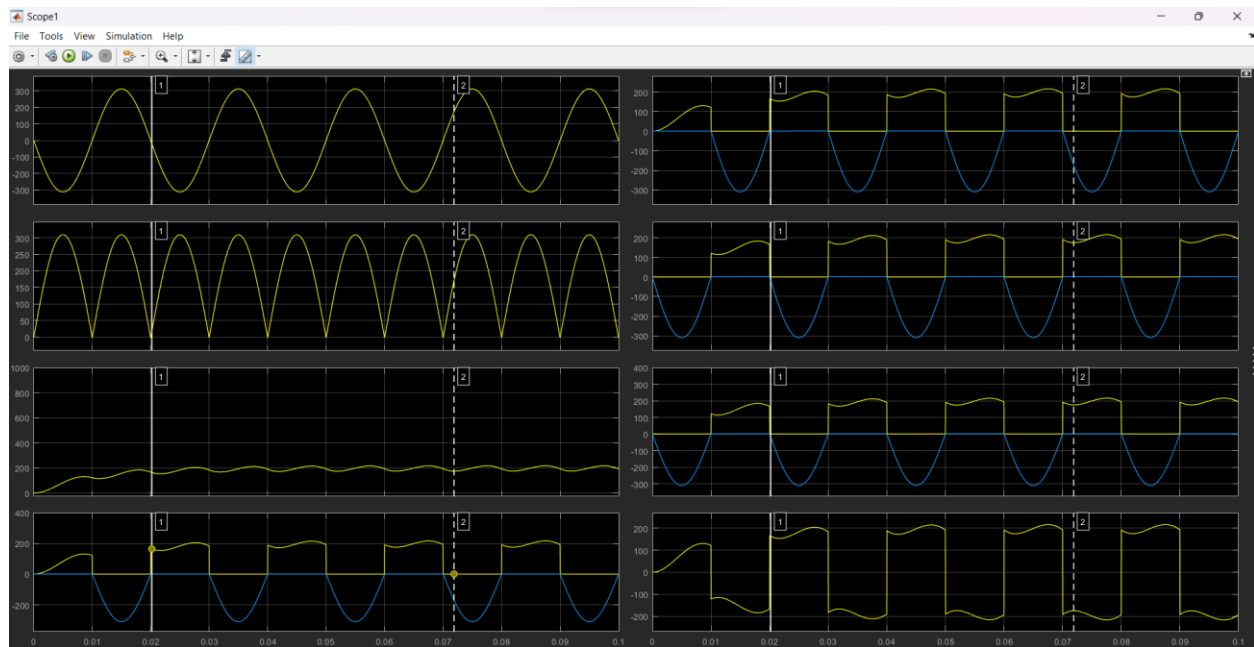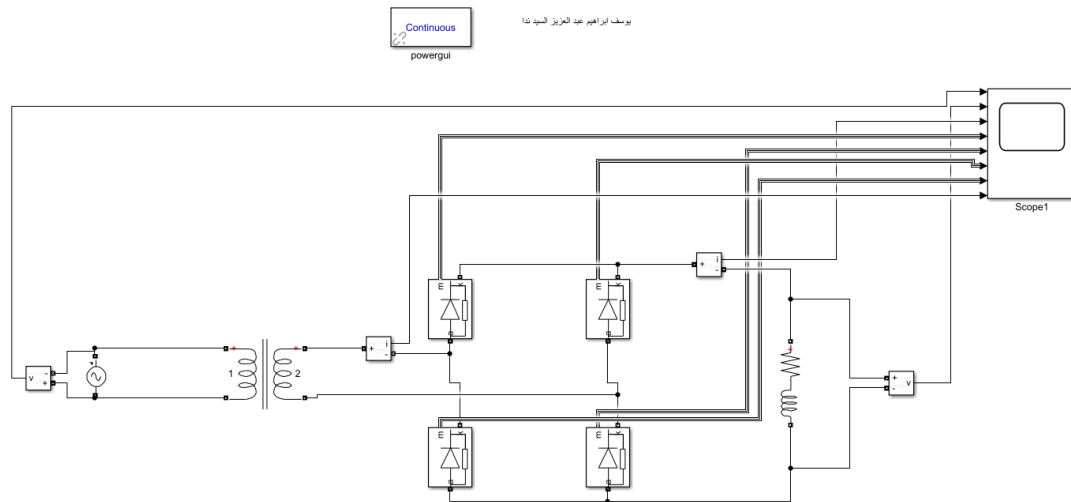
## Single phase Full wave rectifier: Bridge $\rightarrow$ R&L\_load (Highly Inductive)





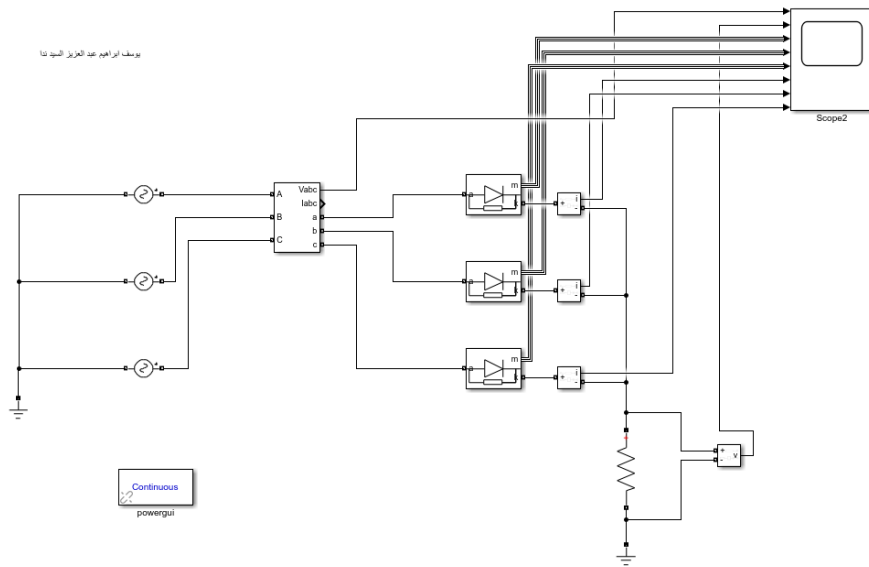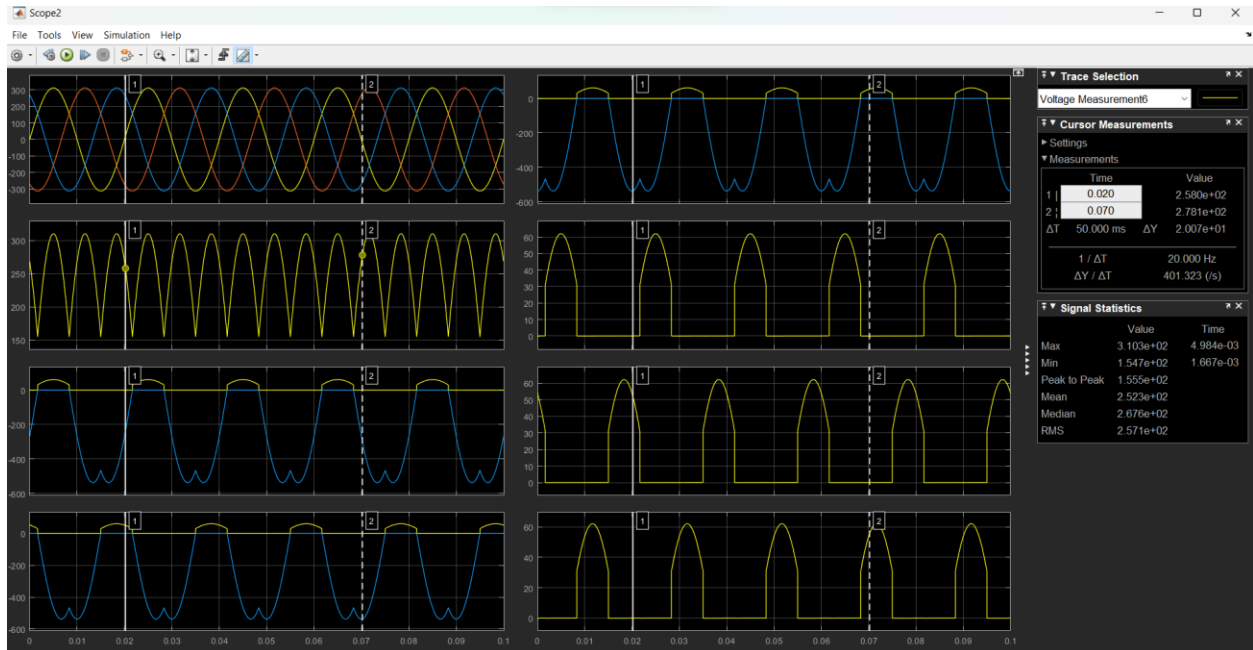Three phase Half wave rectifier → R\_load:







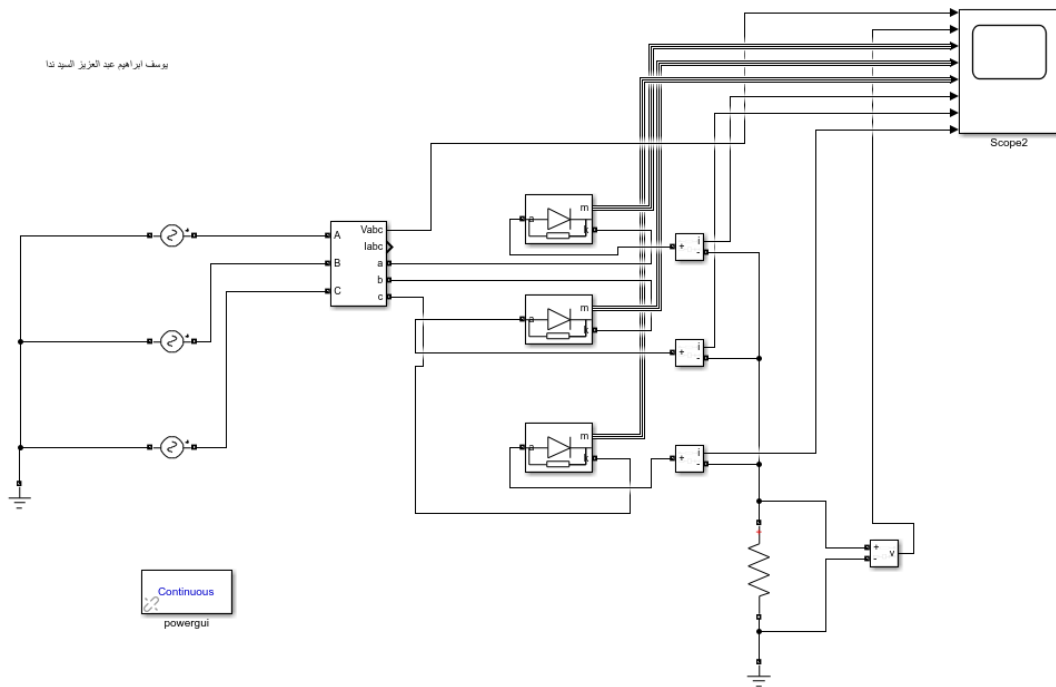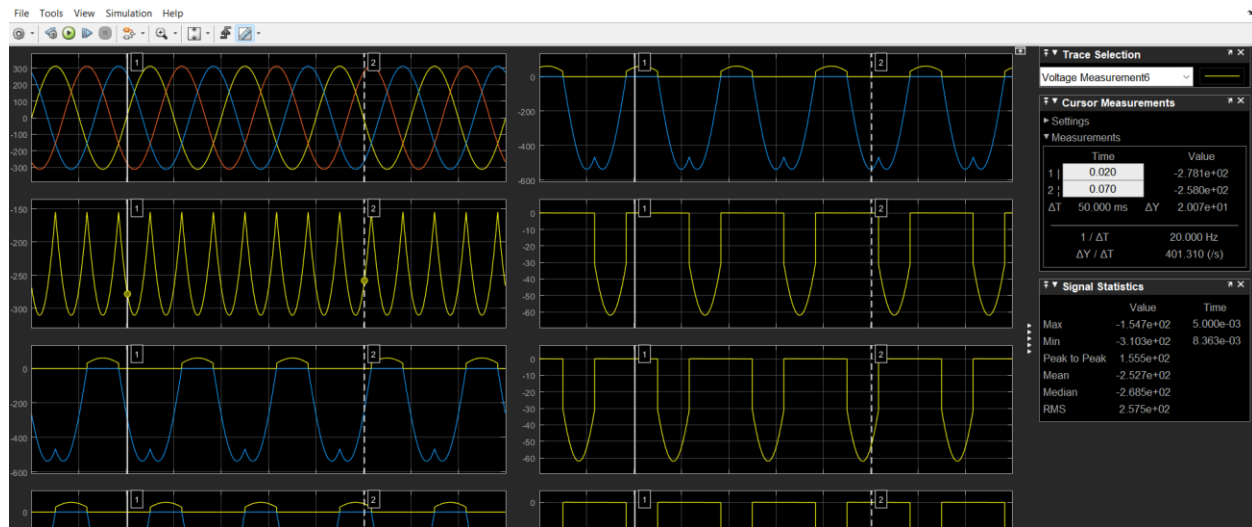
# Three phase Half wave rectifier → R\_load (Reversed):



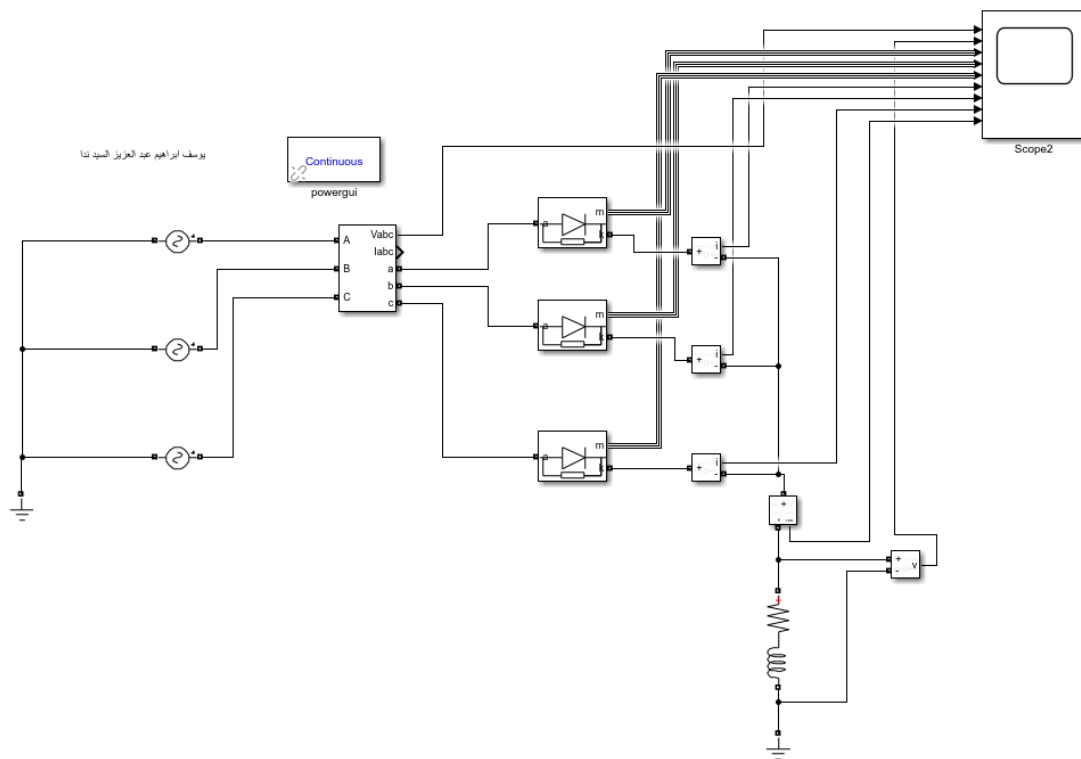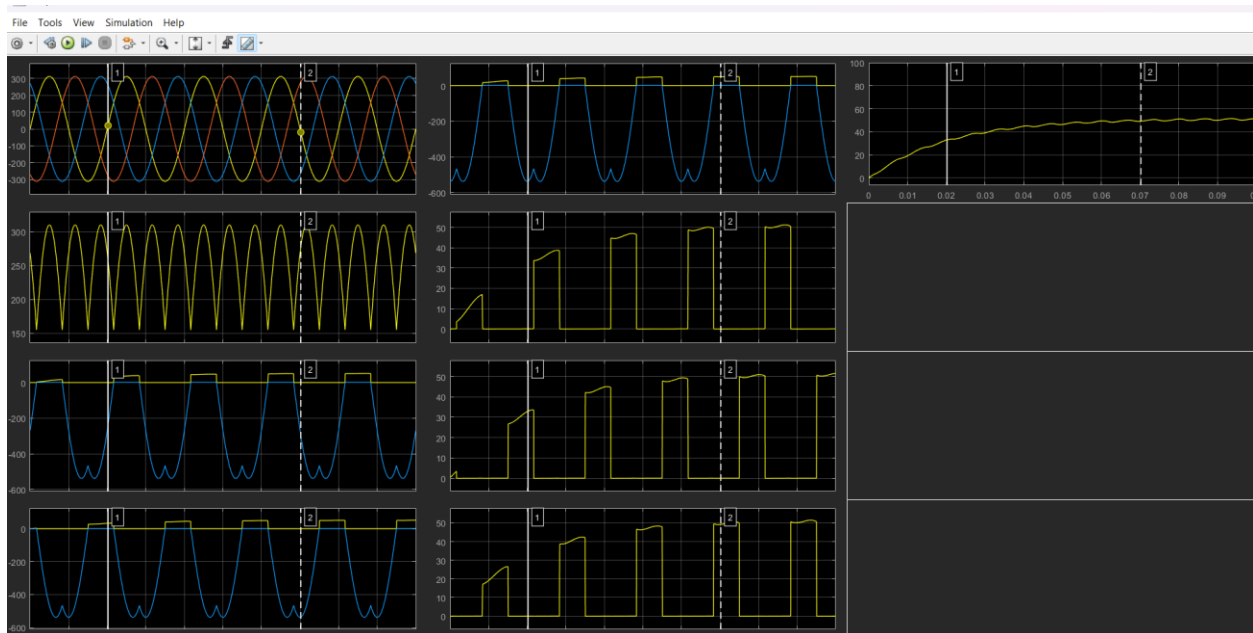
Three phase Half wave rectifier → R&L\_load (Highly Inductive):


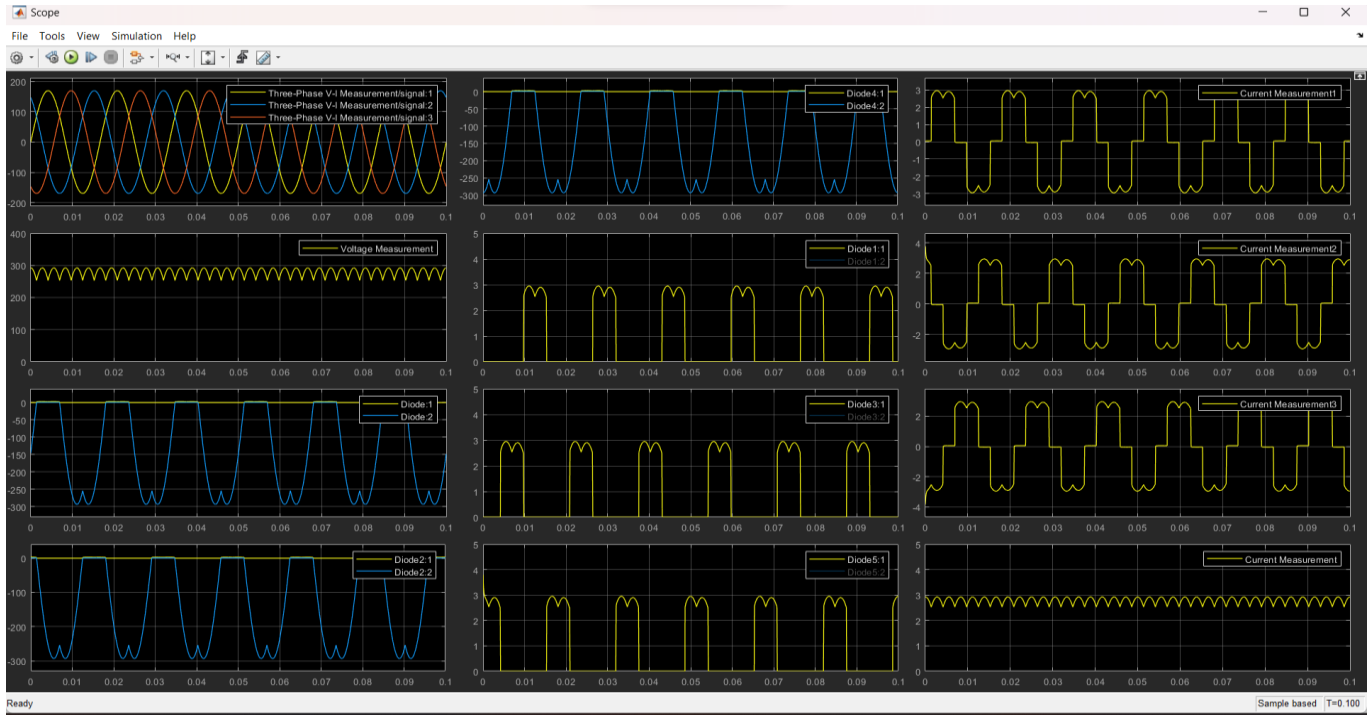
## Three phase Full wave rectifier → (Bridge) R\_load:



يوسف ابراهيم عبد العزيز السيد ندا

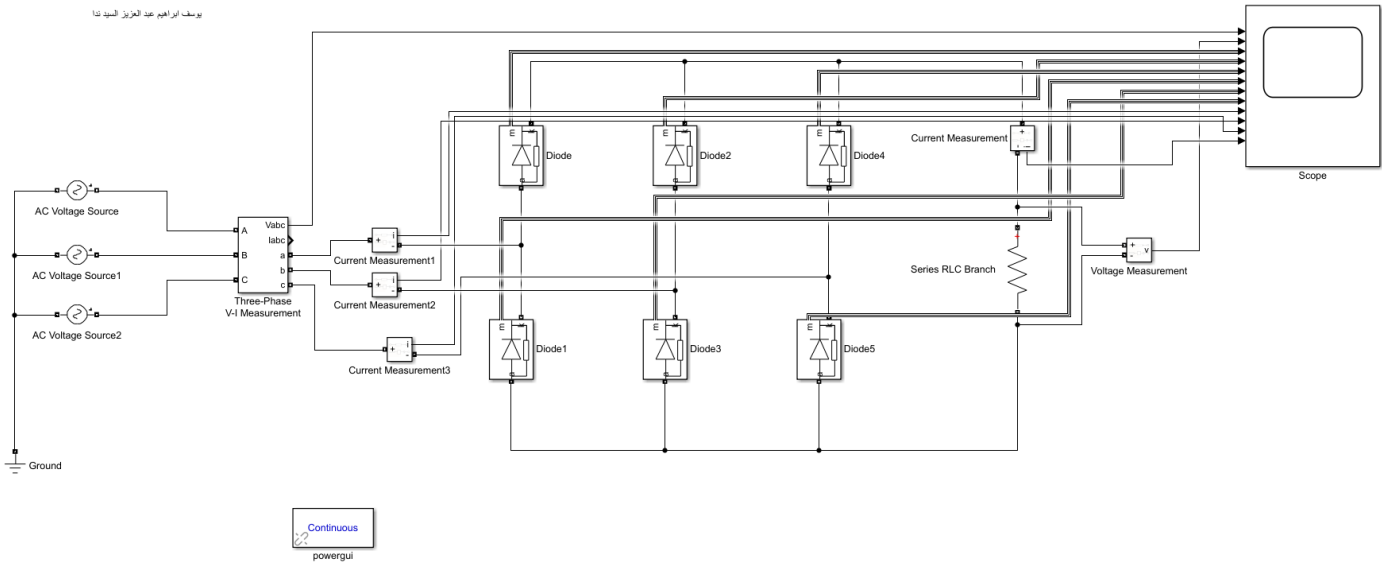

## Three phase Full wave rectifier → (bridge) R&L\_load:

